

Normally I was trying with  $4k7\Omega$  resistors but I change some  $47k\Omega$ s so input doesn't sink more current. Should not matter anyway. Ampere values are as low as  $1mA$  on ampere paths when supply is  $5V$ . Done it because input can be something else then button later. And so little delayed changed for input-output for rising edge detector like  $100ns$ .

$$\underline{R_x = 1k\Omega \quad C_x = 15p}$$

Red = Trigger(2) of 555

Blue = Output(3) of 555






Stop



22-09-13 10:11:47

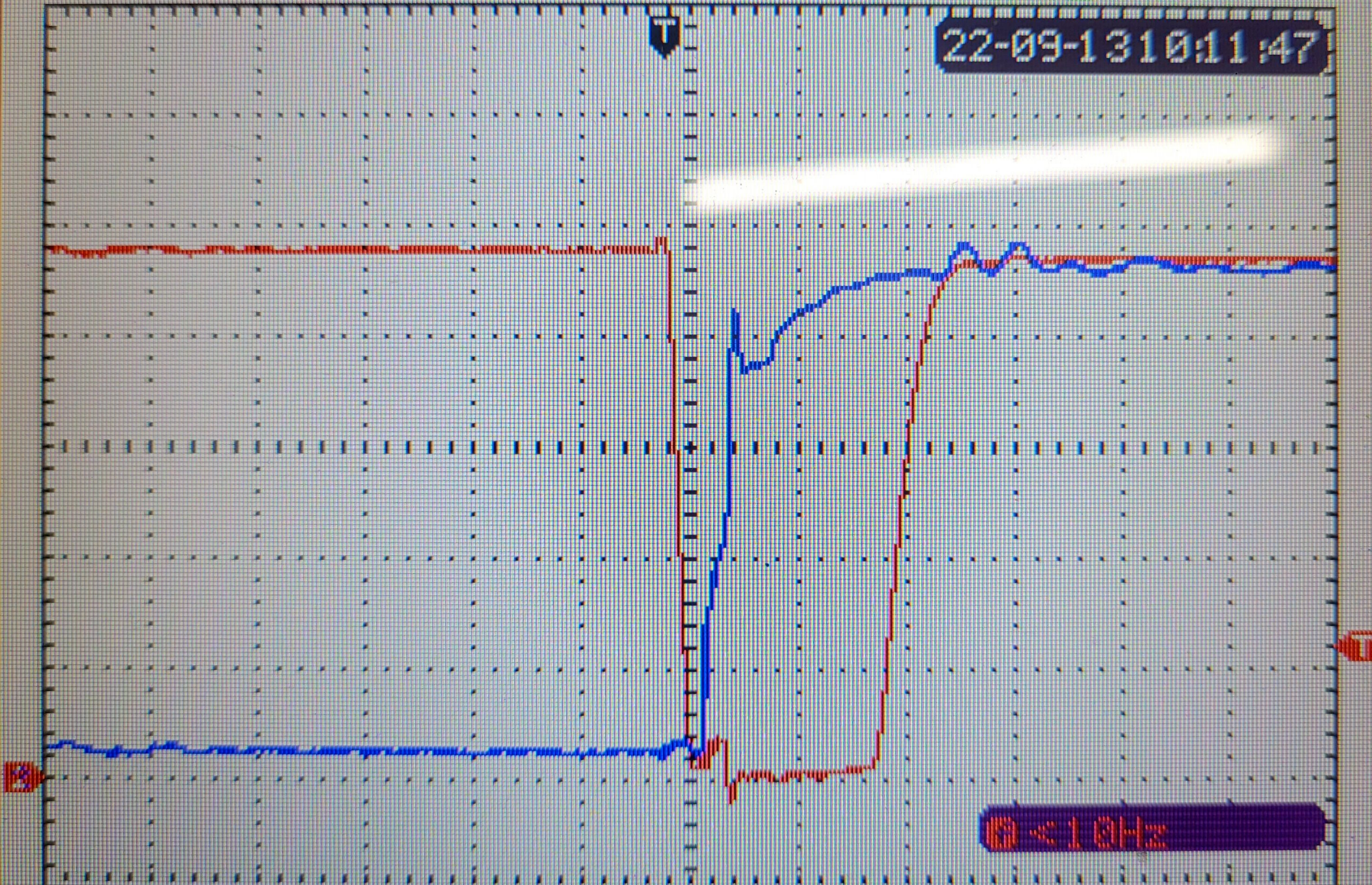

CH1= 1.00V

CH2= 1.00V

M 1.00μs




CH2 X1.20V

M Pos: 210.0ns


0 < 10Hz



STOP

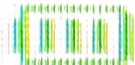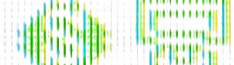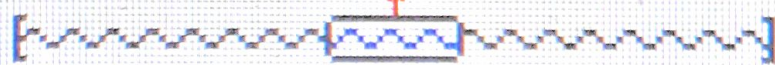

22-09-13 10:12:21

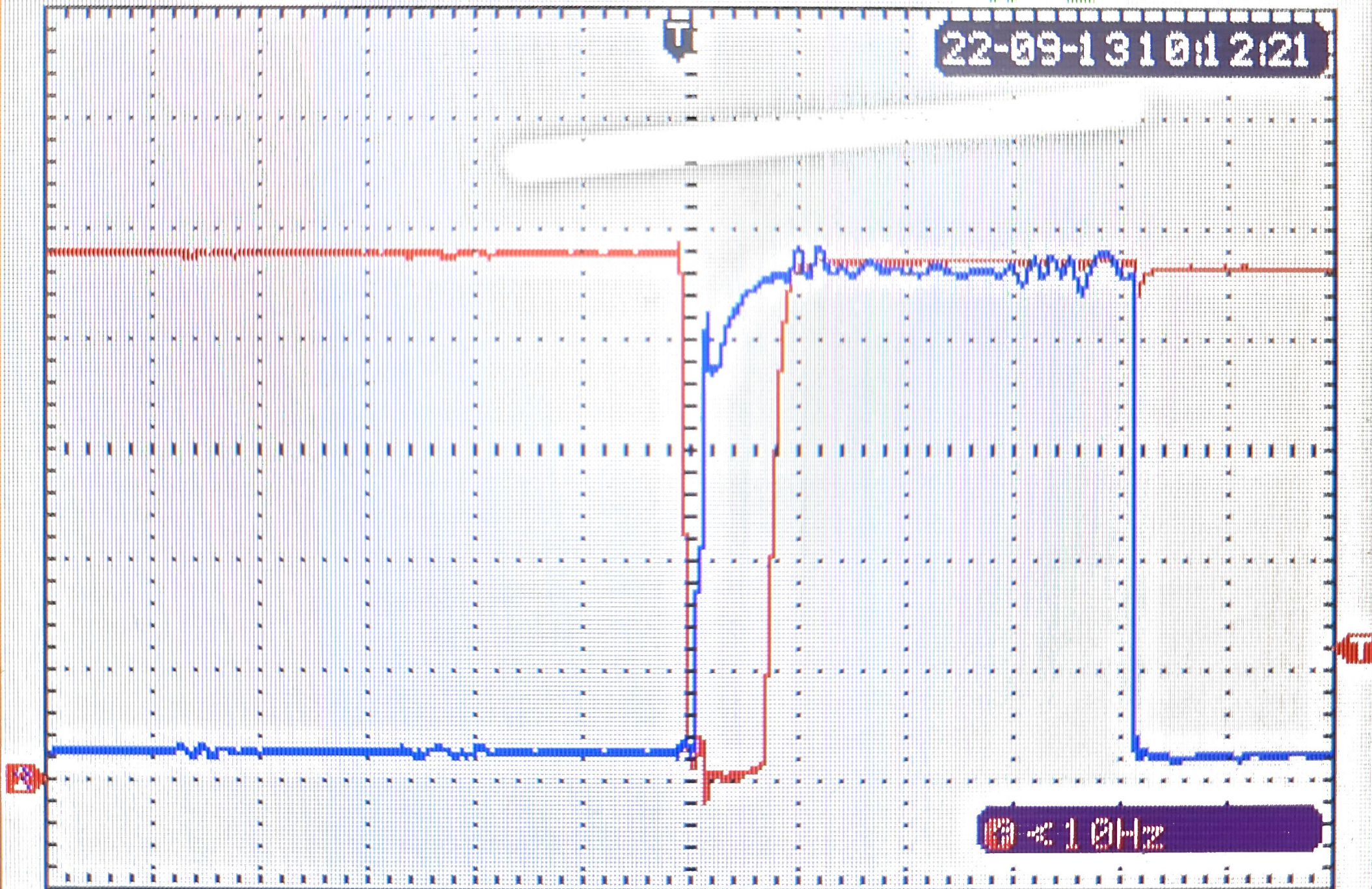

CH1= 1.00V

CH2= 1.00V

M 2.50  $\mu$ s

CH2 X1.20V

M Pos: 210.0ns