

reaction times of not gate on 555 circuit

High to low $\rightarrow 400\text{ns}$
low to high $\rightarrow 20\mu\text{s}$



(output high to low or low to high)

with buttons and just not gate (the same)

previous page circuits and photo numbers

④ high to low $\rightarrow 10\text{ns}$

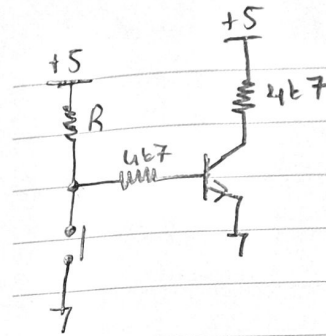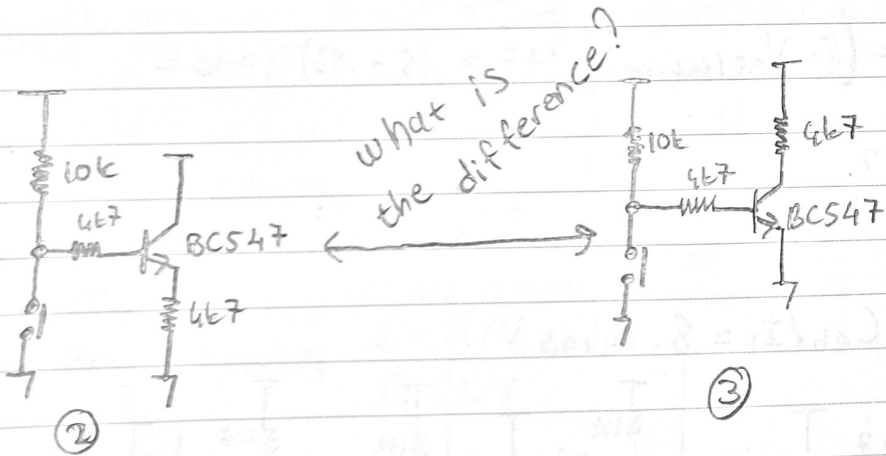③ low to high $\rightarrow 1.1\mu\text{s}$



$R = 100 \rightarrow$ no difference

$R = 82\text{k} \rightarrow$ photo ⑤ no delay

$R = 20\text{k} \rightarrow$ nd

$R = 30\text{k}$

R reaction time of output

10k 1.15-1.44 μs

20k .970-1.1 μs

30k 670-740ns

40k 590-650ns sometimes 1.5 μs



50k 550-950ns

60k 460-650ns

70k 440ns

80k

220k 200-300ns

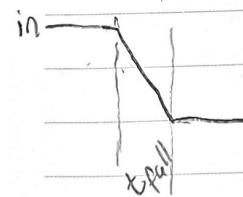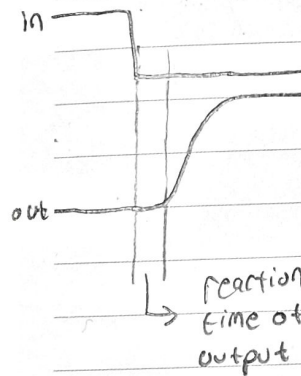

$R = 10\text{k} \rightarrow 20\text{ns}$

$R = 82\text{k} \rightarrow 20\text{ns}$

I pull down with button

but, just curiosity

so it wasn't the delay of the transistor it was about circuit. this is why I didn't need to put capacitance after the not gate of rising edge detector.