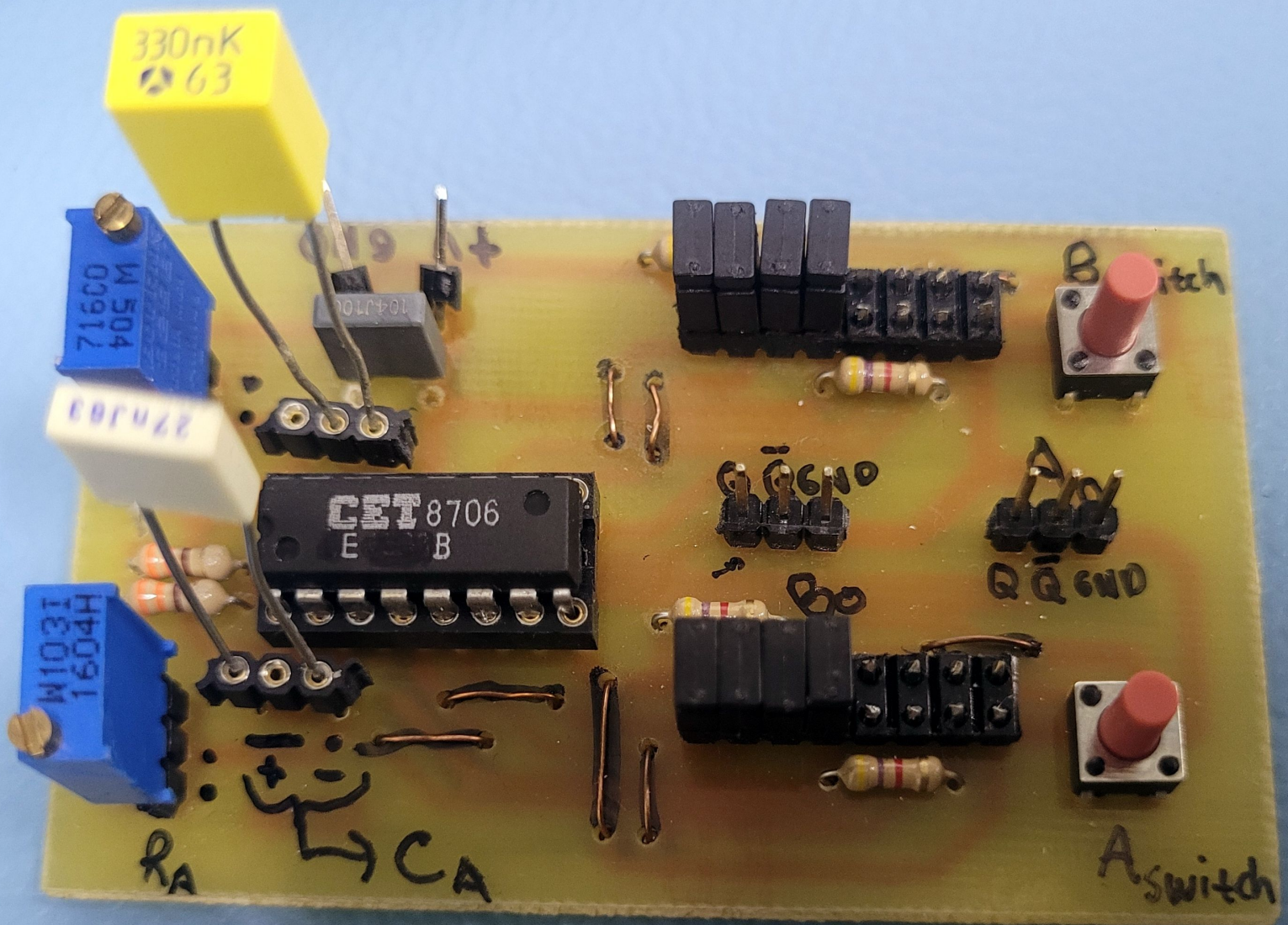


!! Purpose of the jumpers was changeable rising, falling edge inputs. But, I forgot to change input pins with jumpers. Board was intended to use as a single pulse generator module with buttons and later adding physical male or female pins to input pins so single pulse could be both controlled with a signal and buttons. In this situation, board works x2 single pulse generator with rising edge detection.





ON 9

104J100

104J100

CET 8706  
E B

104J100

CA

104J100

104J100

104J100

Q Q 6ND

Q Q 6ND

Q Q 6ND

104J100

104J100

104J100

B switch

B switch

A<sub>0</sub>

Q Q 6ND

Q Q 6ND

A switch

A switch